



ELE1204: Digital Electronics and Logic Design

Lecture 03 (BSCS)

Topic/Theme, e.g., *Combinational Logic Design*

Ms. Olivia Nakayima

(MSc, BSc. CCNA, JNCIA, JNCIS)

Department of Computing & Technology

Faculty of Engineering, Design & Technology

Mon 16th October 2023



Lecture Objectives and Learning outcomes

The Objectives of this lecture are :

- ☐ To understand the combinational circuits
- ☐ To analyse them and their applications

By the end of this lecture, students should be able to:



- ☐ Define combinational circuits
- ☐ Fully explain the adders, multiplexers, encoders and decoders

NOTE:: SMART = **S**pecific, **M**easurable, **A**chievable, **R**elevant, **T**imebound





Lecture Overview

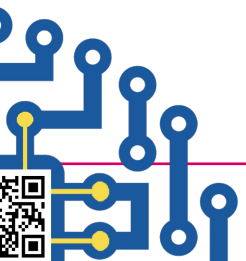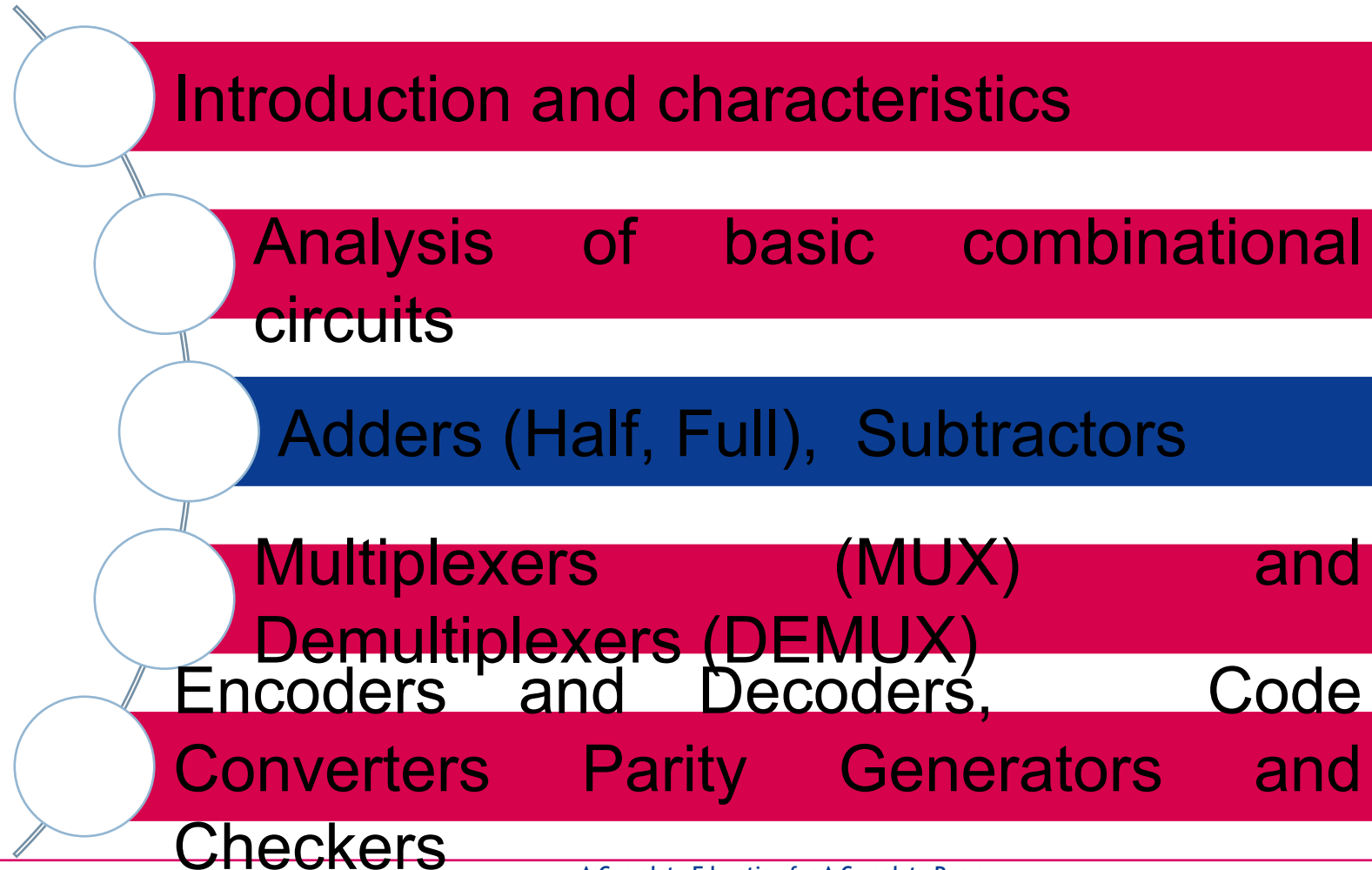

Multiplexers (MUX) and Demultiplexers (DEMUX)

Multiplexer (MUX)

2- to- 1 multiplexer

<https://www.youtube.com/watch?v=FKvnmxte98A>

- A **MUX** selects **one** output from **multiple** inputs based on **select** lines.


Example:

- ❑ **2-to-1 MUX** has **2** inputs (I_0 , I_1), **1** select line (S), and **1** output (Y).


- ❑ When $S = 0$, the upper AND gate is enabled and I_0 has a path to the output. When $S = 1$, the lower AND gate is enabled and I_1 has a path to the output.

- ❑ The multiplexer acts like an electronic switch that selects one of two sources.

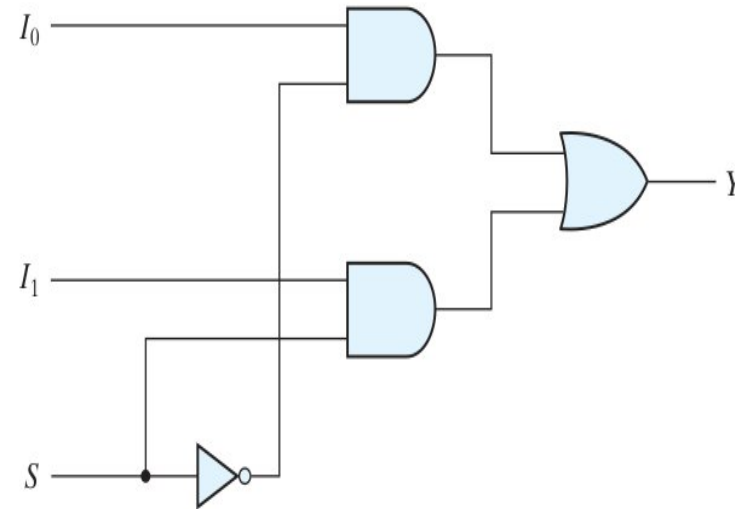- ❑ A multiplexer is also called a data selector, since it selects one of many



(a) Logic diagram

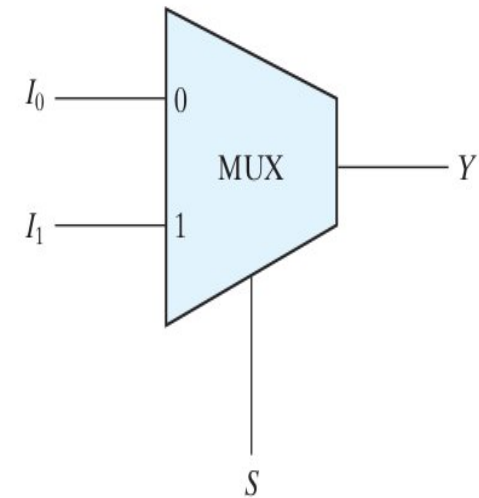


(b) Block diagram

Multiplexers (MUX) and Demultiplexers (DEMUX)

4- to- 1 multiplexer

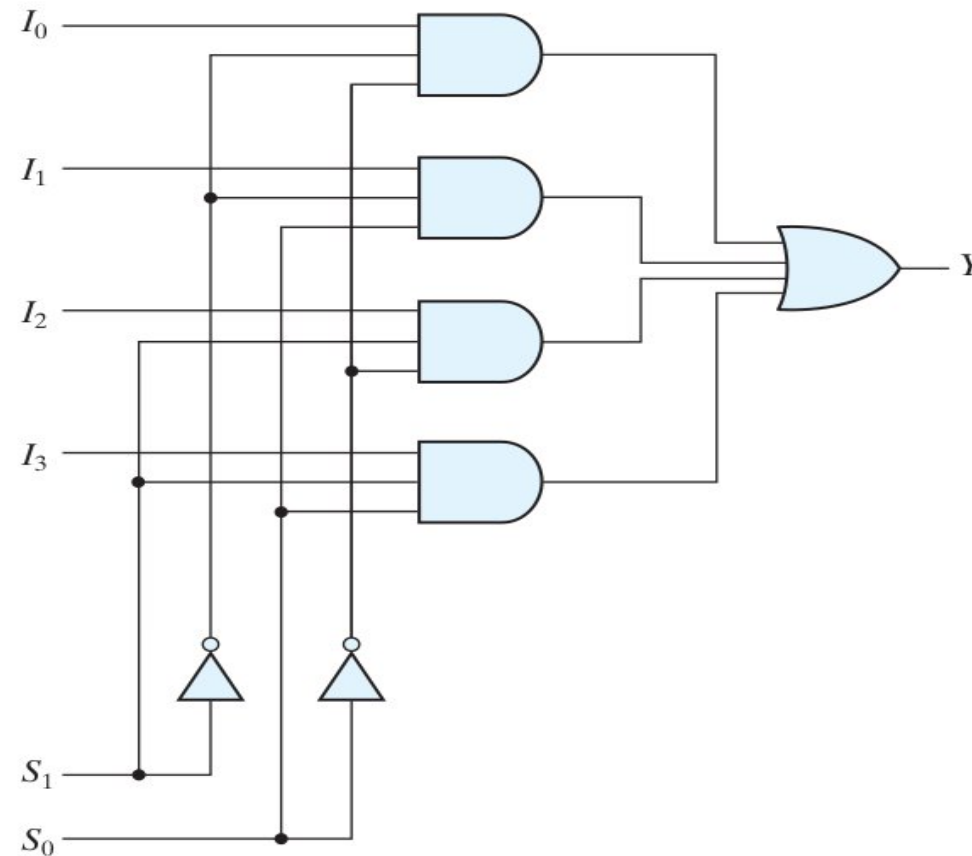- Each of the four inputs I_0 , I_1 , I_2 , and I_3 is applied to one input of an AND gate.
- Selection lines S_1 and S_0 are decoded to select a particular AND gate.
- The outputs of the AND gates are applied to a single OR gate that provides the one-line output



(a) Logic diagram

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table


<https://www.youtube.com/watch?v=g1Lfz1XgrH8>



Multiplexers (MUX) and Demultiplexers (DEMUX)

8 input multiplexer

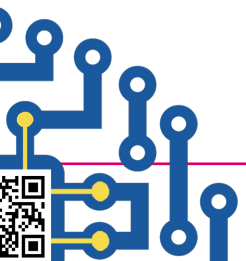- ☐ Has 3 selectors
- ☐ 8 input lines
- ☐ Read about the 8 bit MUX
- ☐ <https://www.youtube.com/watch?v=b0z7YKKCCyY>





Multiplexers (MUX) and Demultiplexers (DEMUX)

Demultiplexer (DEMUX)

- ❑ A **DEMUX** takes **one input** and distributes it to **multiple outputs** based on select lines.
- ❑ Demultiplexer takes one input data source and selectively distributes it to 1 of N output channels just like a multiposition switch
- ❑ The select input code determines to which output the DATA input will be transmitted
- ❑ <https://www.youtube.com/watch?v=t3Ed13z9uz8>

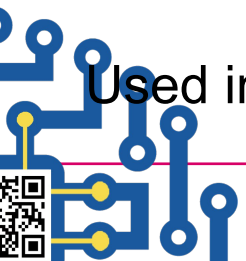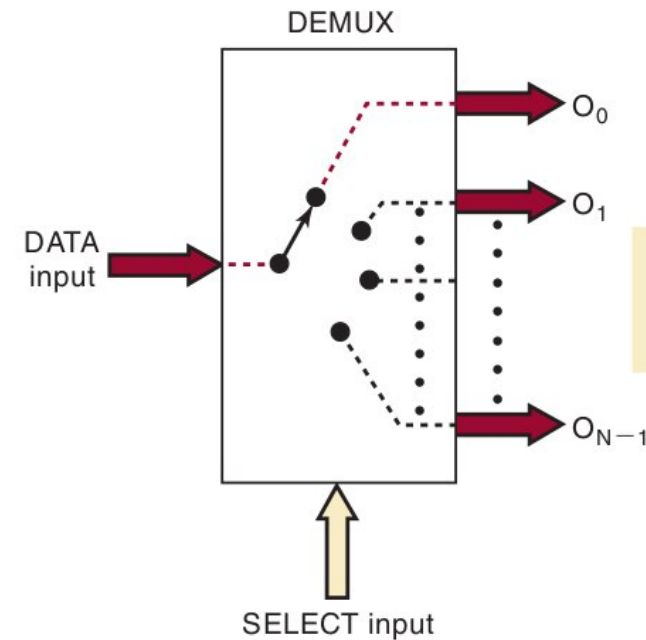Used in **data routing and memory addressing**.





Multiplexers (MUX) and Demultiplexers (DEMUX)

1-line to 8-line Demultiplexer (DEMUX)

Select Code			Outputs							
S_2	S_1	S_0	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0


Note: I is the data input

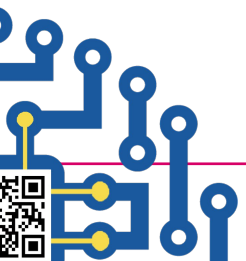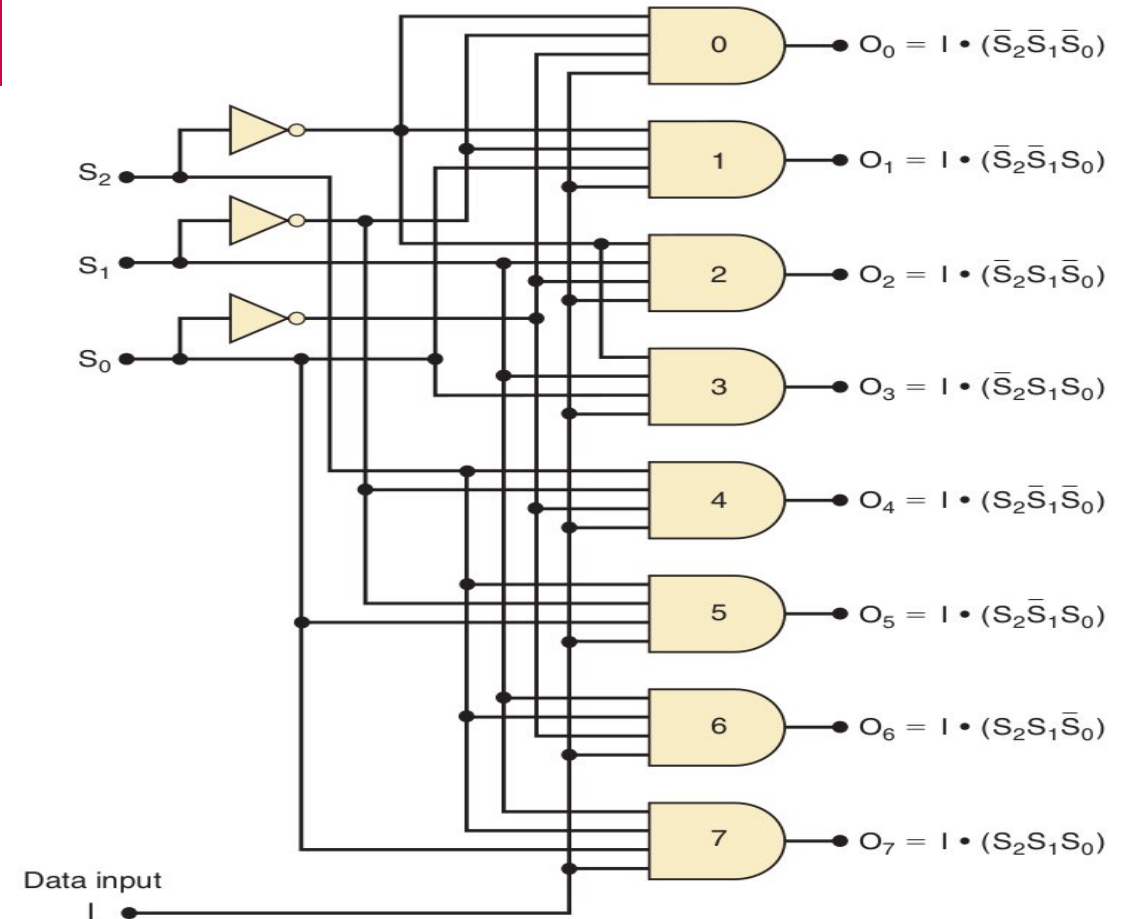

Code Converters, Parity Generators, and Checkers

Code Converters

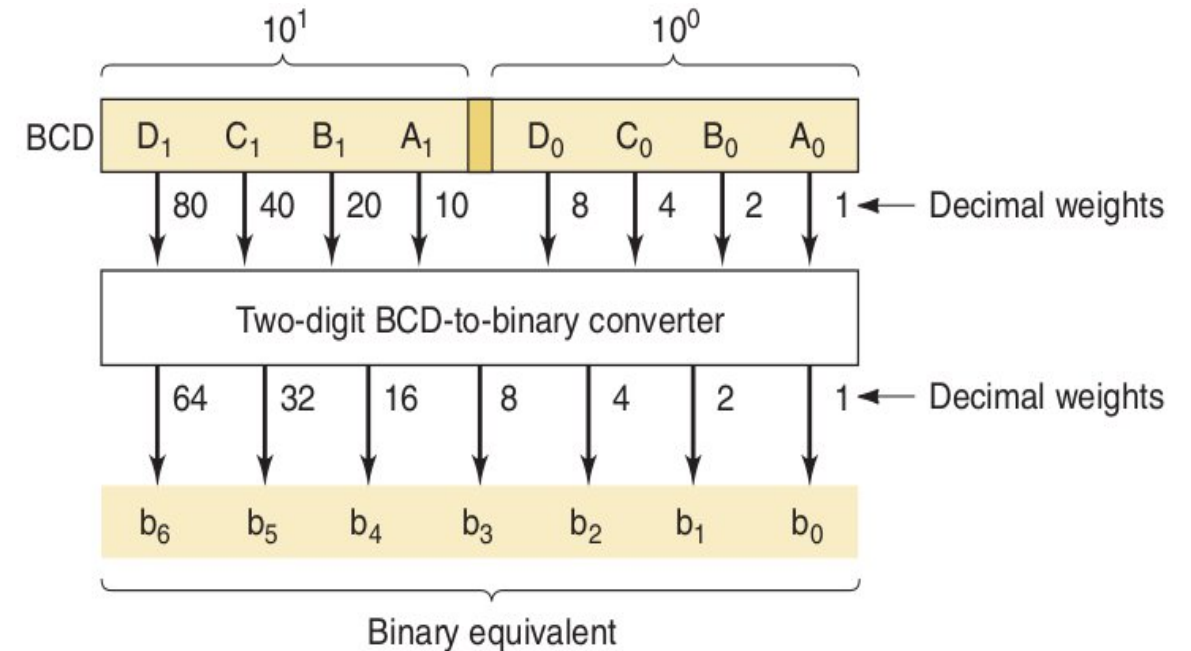- A code converter is a logic circuit that changes data presented in one
- type of binary code to another type of binary code
- **Example: Binary to BCD, Binary to Gray Code.**



Code Converters example

Write down the binary equivalents for all the 1s in the BCD representation. Then add them all together in binary.

<https://www.youtube.com/watch?v=cF-Q5j7RUEw>

1 0 0 1 0 1 0 1 (BCD)


→ 0000001 (binary for 1)

→ 0000100 (binary for 4)

→ 0001010 (binary for 10)

→ + 1010000 (binary for 80)

1011111 (binary for 95)

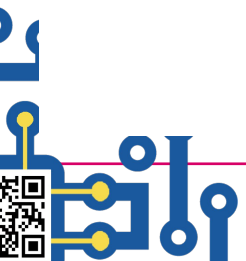

Code Converters, Parity Generators, and Checkers

Parity Generators and Checkers


- ❑ A transmitter can attach a parity bit to a set of data bits before transmitting the data bits to a receiver.
- ❑ **Parity bit** is used for **error detection** in data transmission.
- ❑ **Even parity**: Ensures the number of 1s is even.
- ❑ **Odd parity**: Ensures the number of 1s is odd.

<https://www.youtube.com/watch?v=c8qAti1zBVQ>


BVQ

A Complete Education for A Complete Person

P.O. Box 4, Mukono, Uganda, Plot 67-173, Bishop Tucker Road, Mukono Hill | Tel: +256 (0) 312 350 800 Email: info@ucu.ac.ug Web: <https://ucu.ac.ug>
Founded by the Province of the Church of Uganda. Chartered by the Government of Uganda

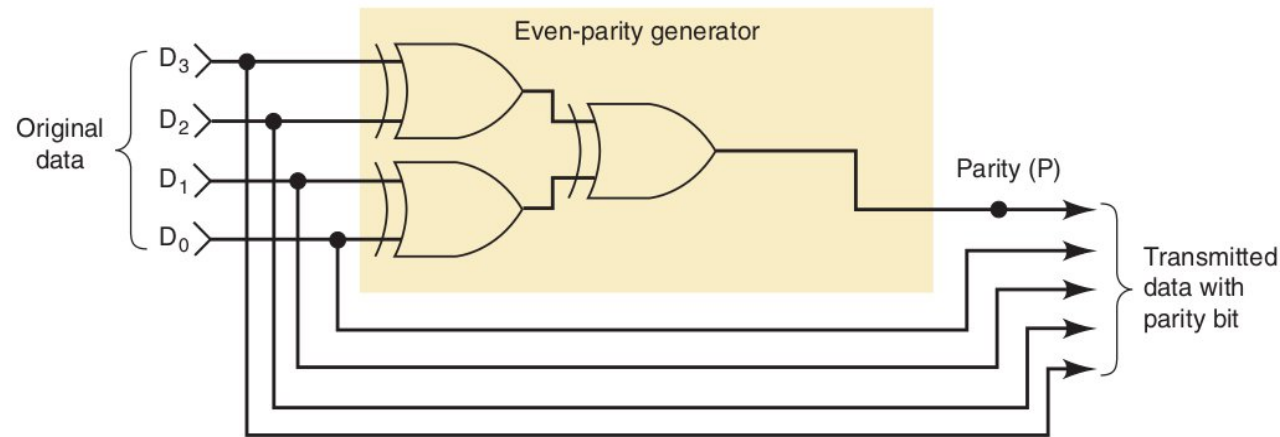

(a)

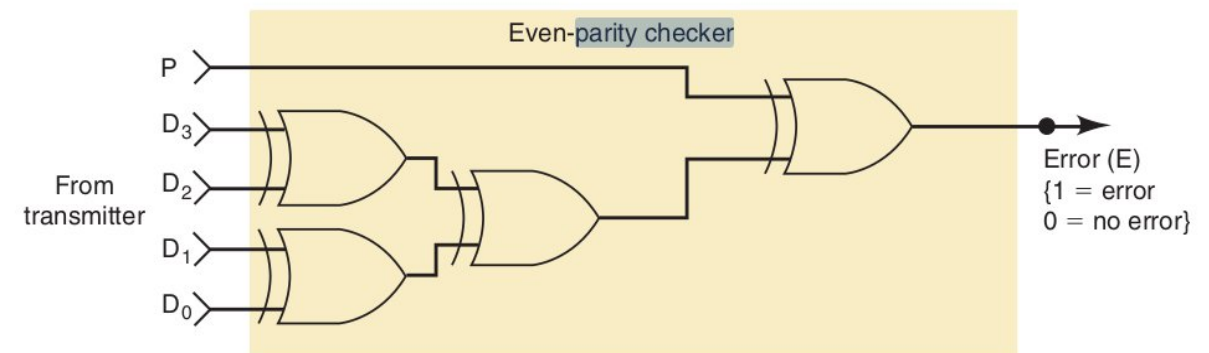

(b)



UGANDA CHRISTIAN
UNIVERSITY

A Centre of Excellence in the Heart of Africa



Uganda Christian University

P.O. Box 4 Mukono, Uganda

Tel: 256-312-350800

 <https://ucu.ac.ug/> Email: info@ucu.ac.ug.

 @ugandachristianuniversity  @UCUniversity

 @UgandaChristianUniversity



Department of Computing & Technology FACULTY OF ENGINEERING, DESIGN AND TECHNOLOGY

Tel: +256 (0) 312 350 863 | WhatsApp: +256 (0) 708 114 300

 @ucuc Computeng  @ucu_ComputEng

 <https://cse.ucu.ac.ug/> Email: dct-info@ucu.ac.ug

A Complete Education for A Complete Person

P.O. Box 4, Mukono, Uganda, Plot 67-173, Bishop Tucker Road, Mukono Hill | Tel: +256 (0) 312 350 800 Email: info@ucu.ac.ug Web: <https://ucu.ac.ug>

Founded by the Province of the Church of Uganda. Chartered by the Government of Uganda